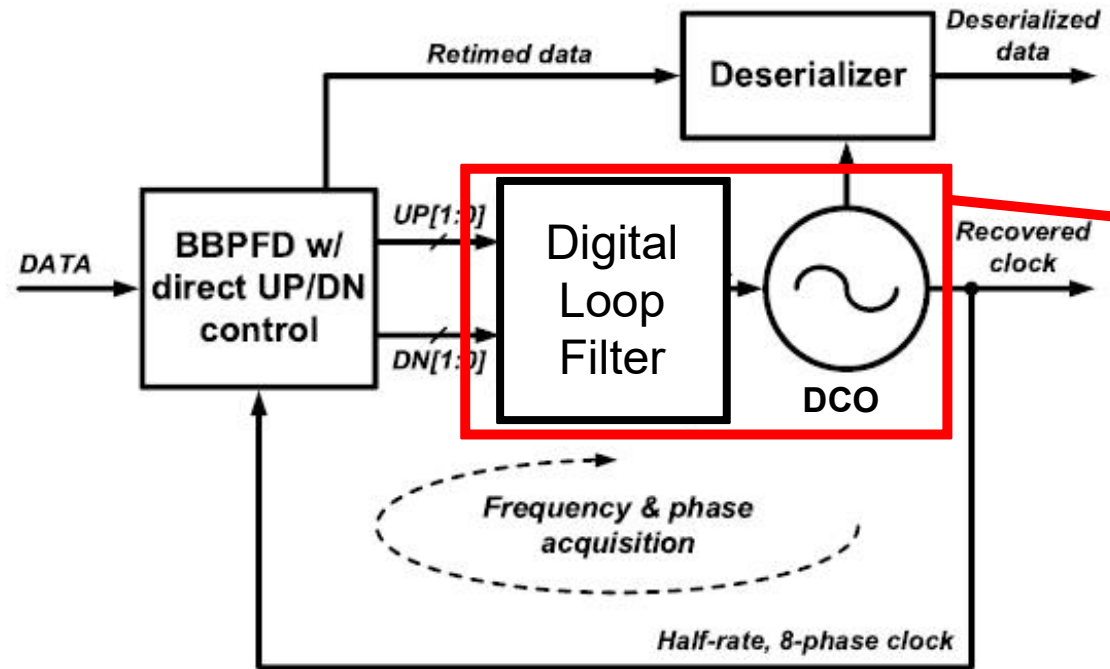


Referenceless Digital Clock Data Recovery with counter-based Kp/Ki Control

EECS, SNU
2017-19047
Sungyoung Lee

Brief Refresher

- Referenceless Digital CDR




- Dithering is unavoidable

KEY GOAL of CALIBRATION :
minimizing the recovered clock's
phase dithering step

Fig. 10. Proposed referenceless CDR block diagram.

Brief Refresher

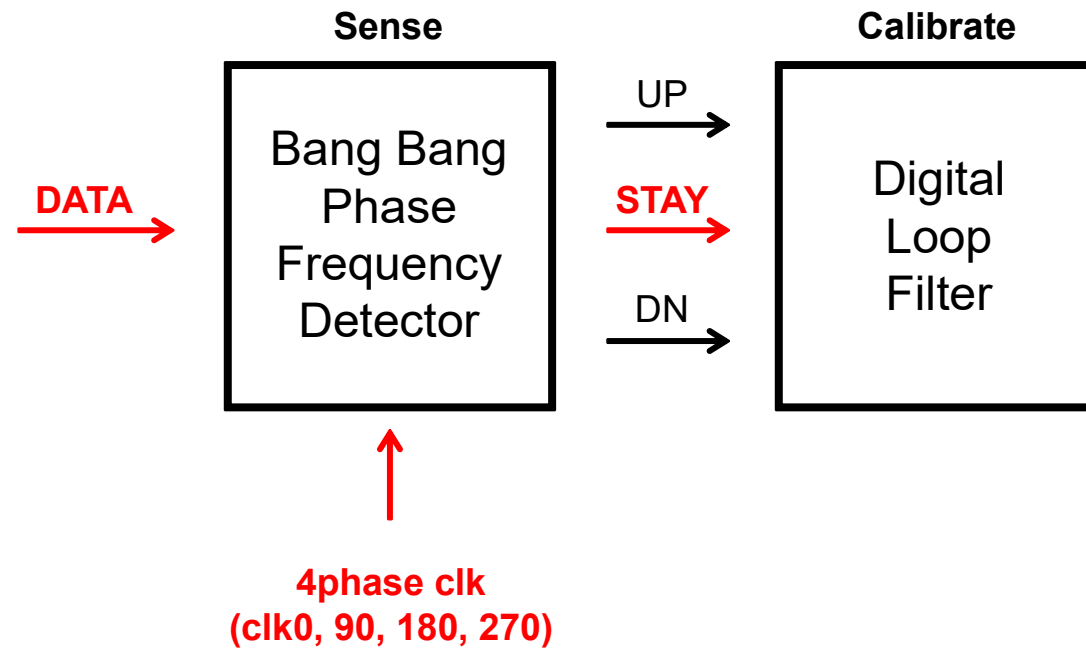
- Sensing & Calibrating DCO Dither (Proposal)



Architecture

Overall Architecture

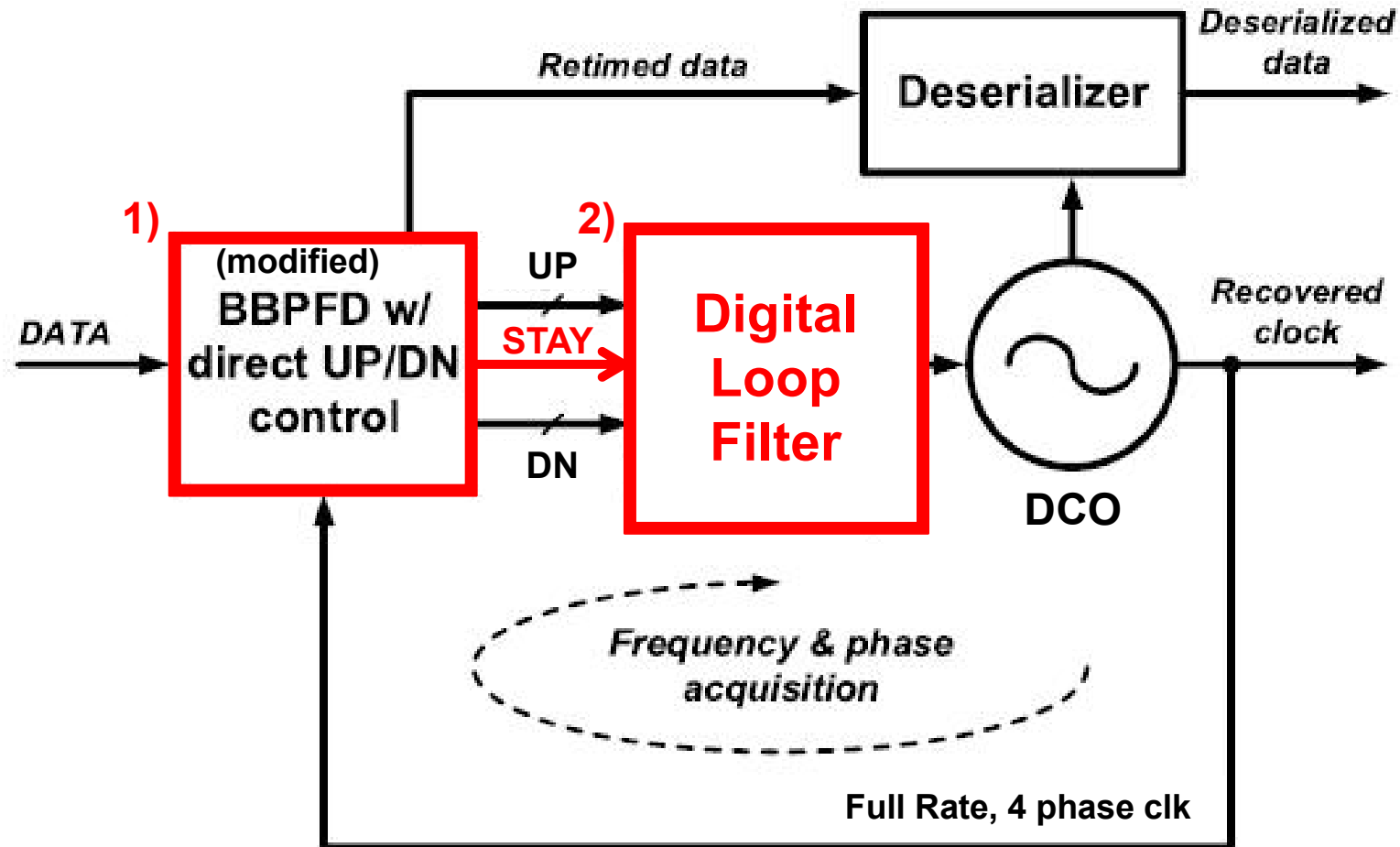- Proposing Referenceless Oversampling Digital CDR




1) Bang Bang Phase Frequency Detector

- Sensing STAY signal

At Successfully Locked Condition :

 data is always sampled(clk0) within this range with this method



Data


CLK₀

CLK₁₈₀

data sampling clk


CLK₉₀

CLK₂₇₀

 


a : data value sampled at CLK₉₀
b : data value sampled at CLK₂₇₀

a == b

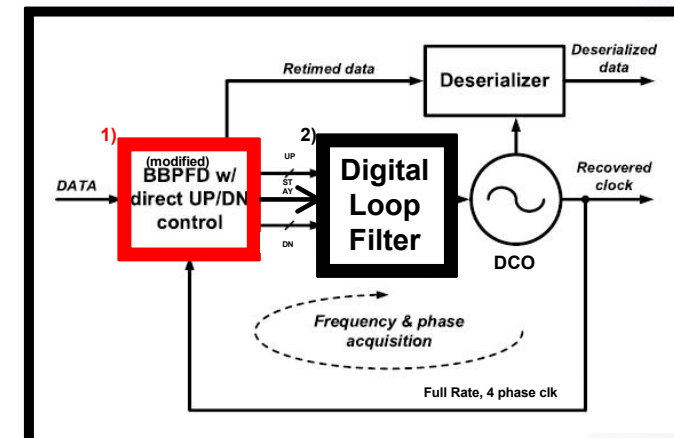


1) Bang Bang Phase Frequency Detector

- Sensing STAY signal


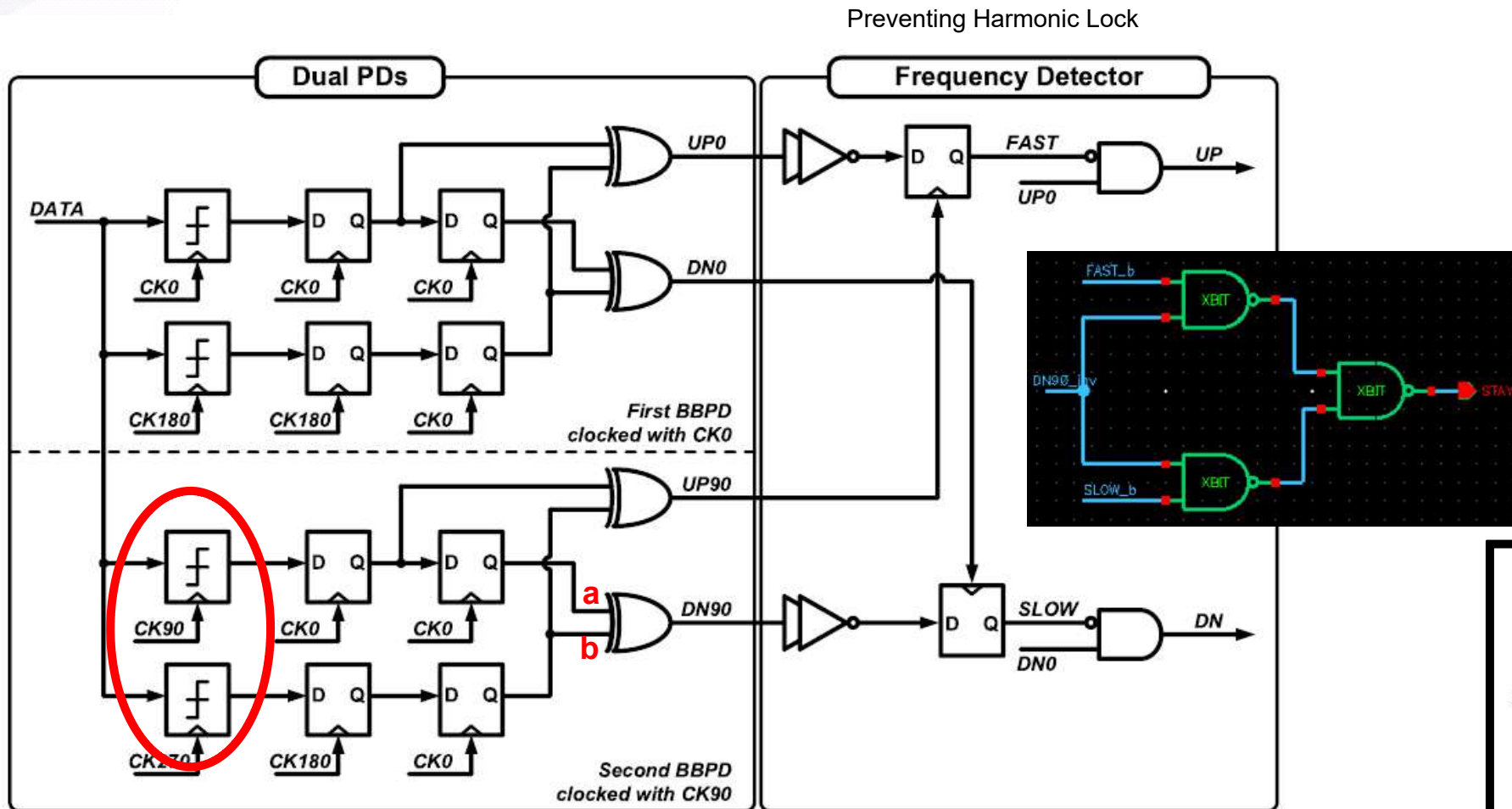

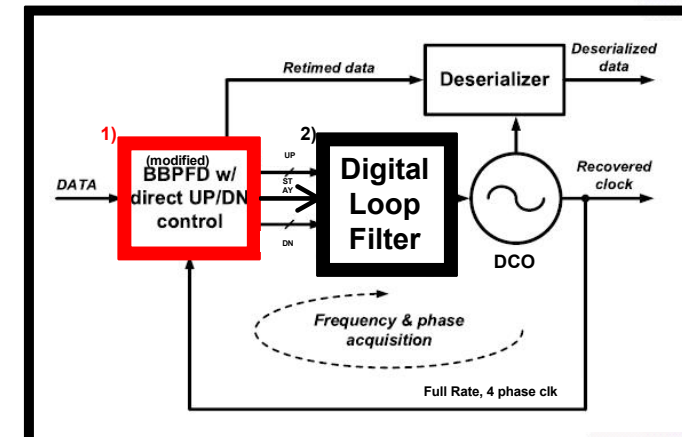
$$(a == b) \text{ \& } (FAST \text{ \& } SLOW == 0) : STAY = 1$$





2) Digital Loop Filter

- Calibrating without STAY signal

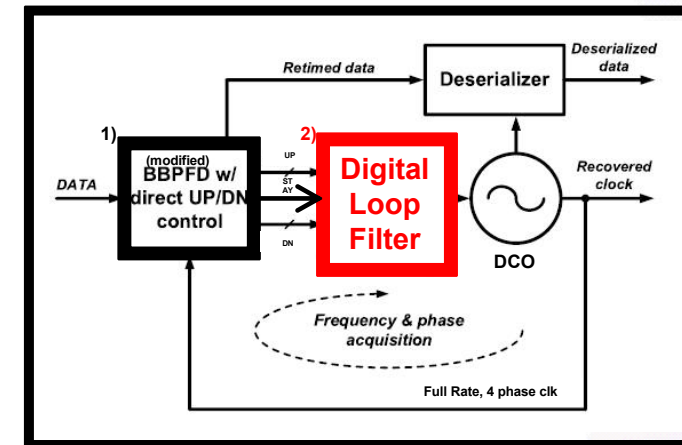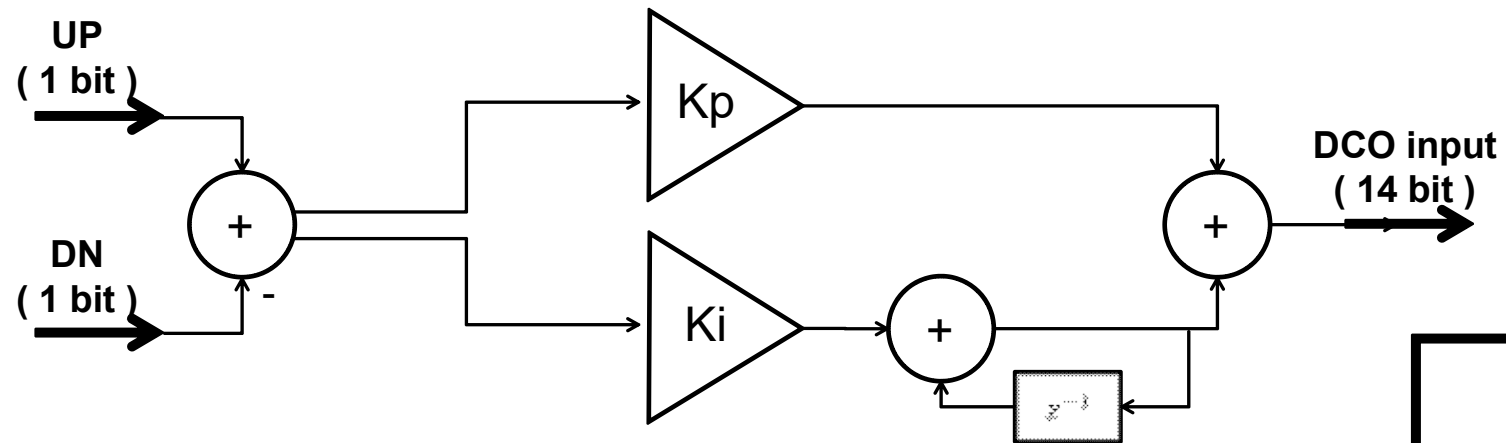

2) Digital Loop Filter

- Calibrating with STAY signal

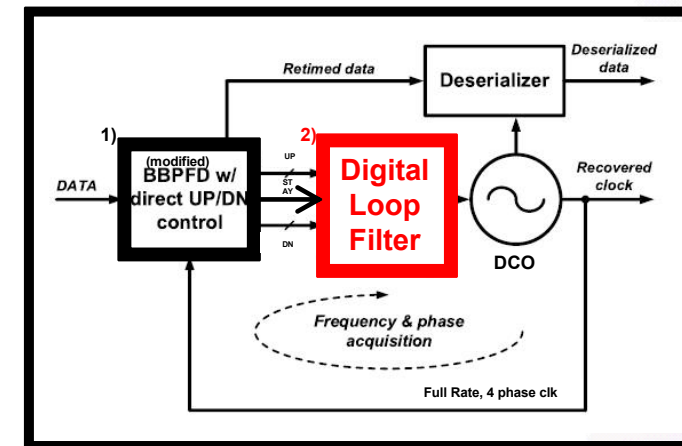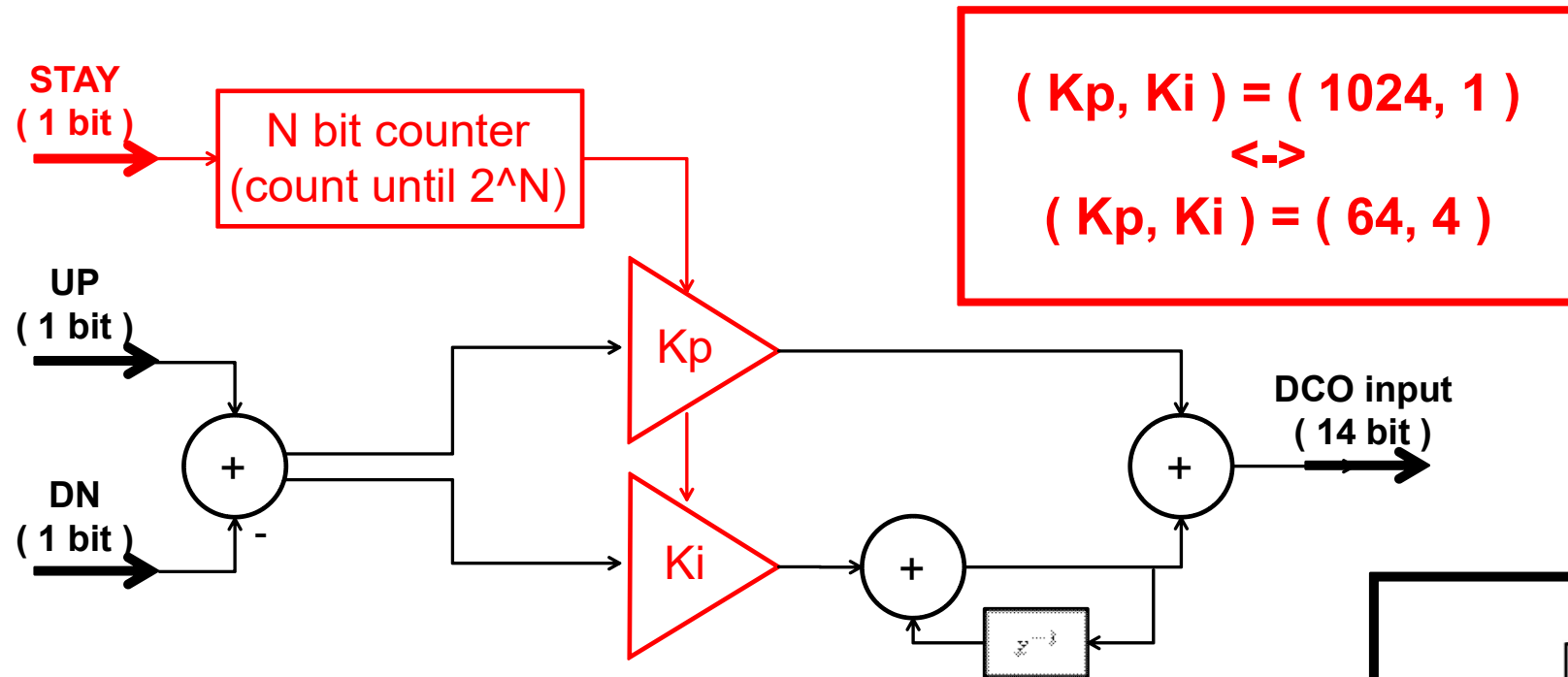

2) Digital Loop Filter



- Calibrating with STAY signal (XMODEL)

```
module digital_lf_z2 #(
    parameter integer(width_out,12), // width of out
    parameter integer(Nd,4), // loop filter delay
    parameter bit([width_out-1:0]init_out,12'b100000000000), // initial out
    parameter integer(Kp,1024), // proportional gain
    parameter integer(Ki,1), // integral gain
    parameter integer(Kp_locked,256), // proportional gain when locked
    parameter integer(Ki_locked,4), // integral gain when locked
    parameter integer(log_Ns,8) // count stay signal for 2^Ns times
)()
    output reg [13:0] out, // output signal
    input bit clk, // triggering clock
    input bit up, // up signal from pfd
    input bit dn, // down signal from pfd
    input bit stay // stay signal from pfd

    // variables
    reg [width_out-1:0] out_d [Nd-1:0];
    reg [width_out-1:0] acc;
    reg [width_out-1:0] out_p;
    reg lock;
    reg [log_Ns-1:0] stay_counter;

    int i;

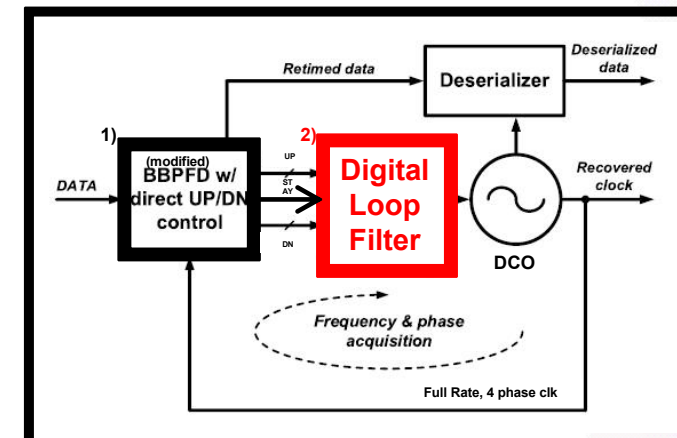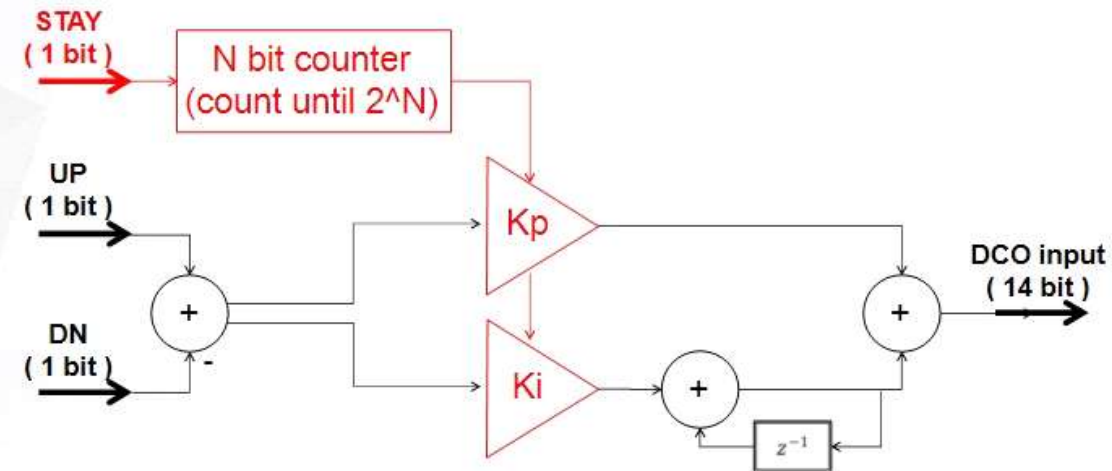    // initialize out
    initial begin
        for (i=0; i<Nd; i++) begin
            out_d[i] = init_out;
        end
        acc = init_out;
        lock = 1'b0;
        stay_counter = {log_Ns{1'b0}};
    end
end
```



2) Digital Loop Filter

- Calibrating with STAY signal (XMODEL)

```

always @(posedge clk) begin
    if (~lock) begin
        acc = acc + Ki*(up - dn); // accumulator for integral path
    end
    if (lock) begin
        acc = acc + Ki_locked*(up - dn); // accumulator for integral path
    end

    // lock
    if (stay) begin
        if (stay_counter == {log_Ns[1'b1]}) begin
            lock = 1;
        end
        else begin
            stay_counter = stay_counter + 1;
        end
    end

    // unlock
    if (~stay) begin
        lock = 0;
        stay_counter = {log_Ns[1'b0]};
    end
end

always @(acc or up or dn) begin
    if (~lock) begin
        out_p = Kp*(up - dn) + acc;
    end
    if (lock) begin
        out_p = Kp_locked*(up - dn) + acc;
    end
end



assign out = out_d[Nd-1];

always @(posedge clk) begin
    for (i=Nd-1; i>0; i--) out_d[i] = out_d[i-1];
    out_d[0] = out_p;
end
endmodule

```

STAY = 1
(N consecutive times)

STAY = 0
(Once)

 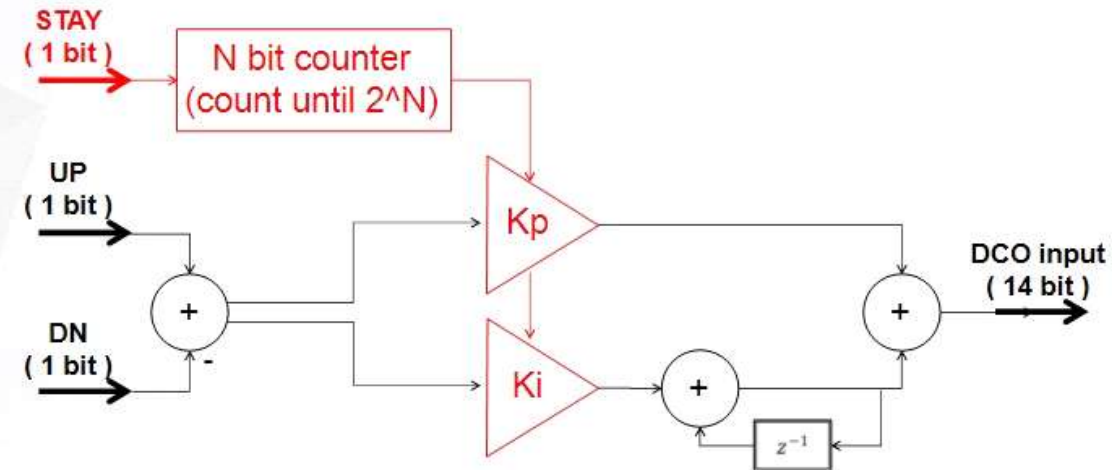

2) Digital Loop Filter

- Calibrating with STAY signal (XMODEL)

```
always @(posedge clk) begin
```

```
    if (~lock) begin
        acc = acc + Ki*(up - dn); // accumulator for integral path
    end
    if (lock) begin
        acc = acc + Ki locked*(up - dn); // accumulator for integral path
    end
```

```
    // lock
    if (stay) begin
        if (stay_counter == {log_Ns{1'b1}}) begin
            lock = 1;
        end
        else begin
            stay_counter = stay_counter + 1;
        end
    end
```

```
    // unlock
    if (~stay) begin
        lock = 0;
        stay_counter = {log_Ns{1'b0}};
    end
```

```
end
```

```
always @(acc or up or dn) begin
```

```
    if (~lock) begin
        out_p = Kp*(up - dn) + acc;
    end
    if (lock) begin
        out_p = Kp locked*(up - dn) + acc;
    end
```



```
end
```

```
assign out = out_d[Nd-1];
```


```
always @(posedge clk) begin
    for (i=Nd-1; i>0; i--) out_d[i] = out_d[i-1];
    out_d[0] = out_p;
end
```

```
endmodule
```

Change Kp, Ki
by lock value

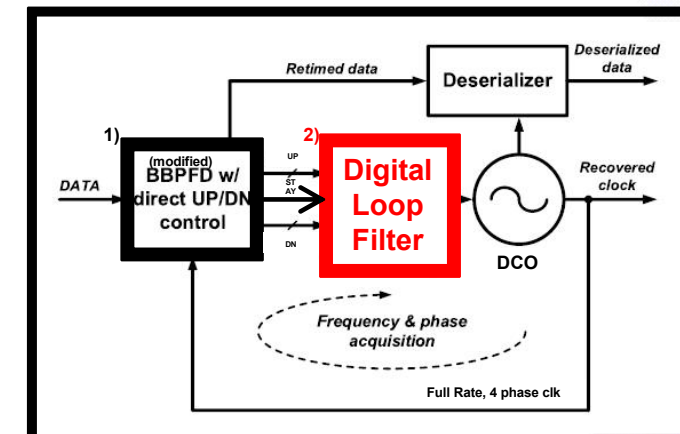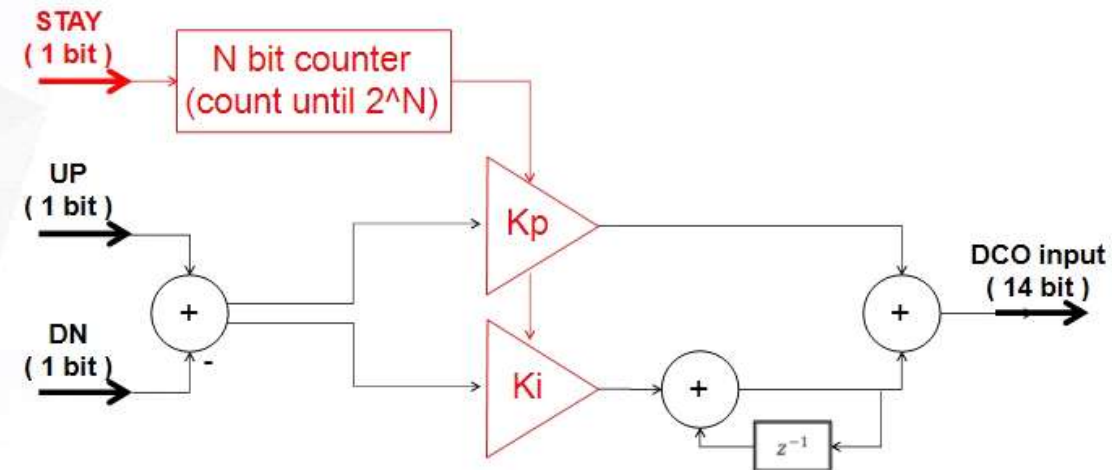

Test Conditions

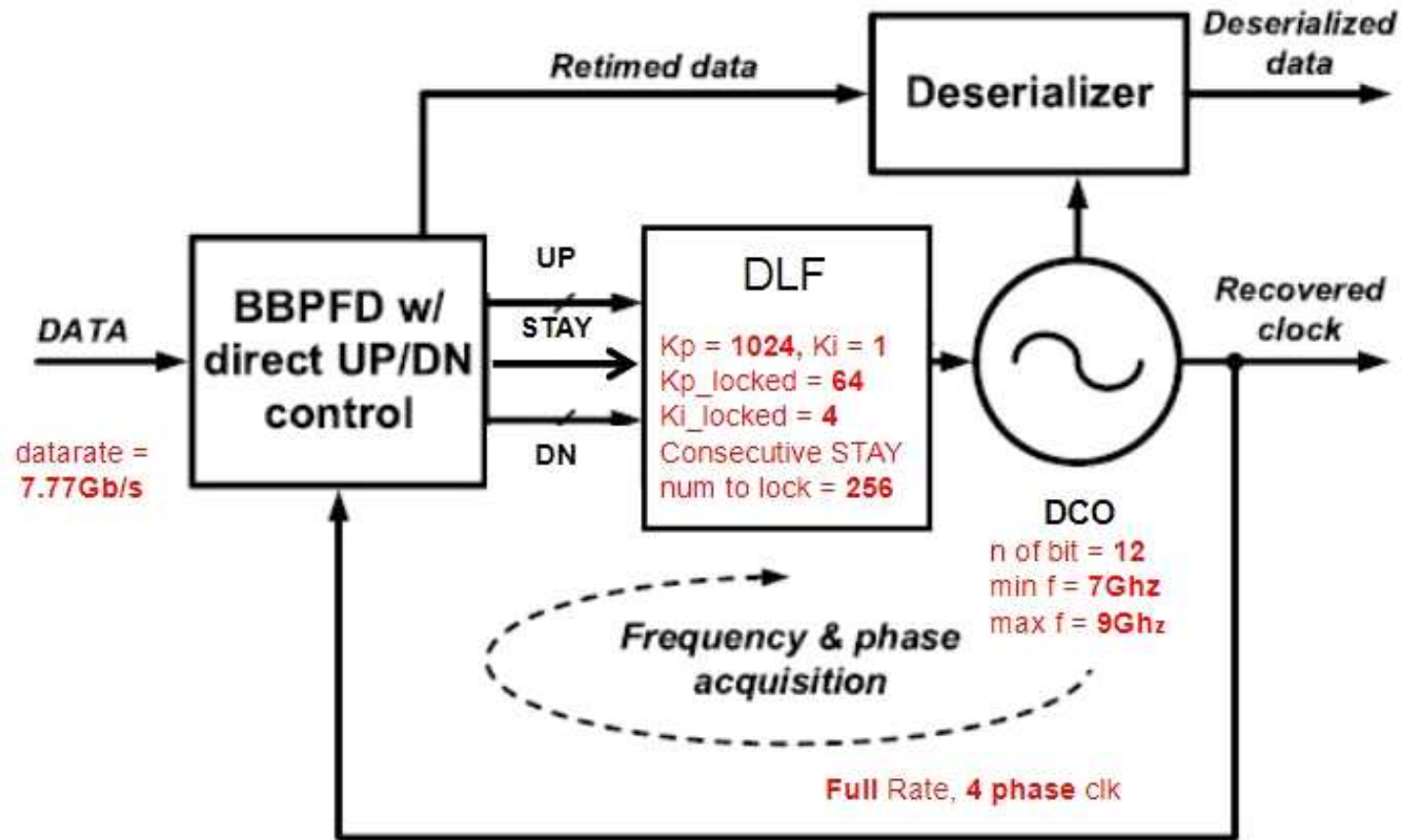

For Analog CDR in phase noise comparison

CP up/dn current = 200uA

Initial Control Voltage = 0.5V

Rs = 0.7k ohm, Cs = 14.4pF, Cp = 3.6pF

VCO range : 7GHz ~ 9GHz

For Digital CDR in functionality and performance comparison

1) Kp = 1024, Ki = 1

2) Kp = 64, Ki = 4


(all the other conditions are same)

Functionality Test

Frequency/Phase of the Recovered Clock


- without STAY signal (K_p, K_i) = (1024, 1)

frequency

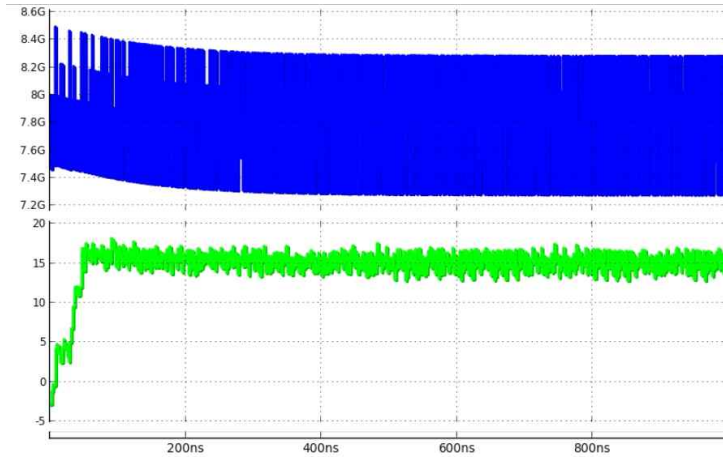

phase


frequency

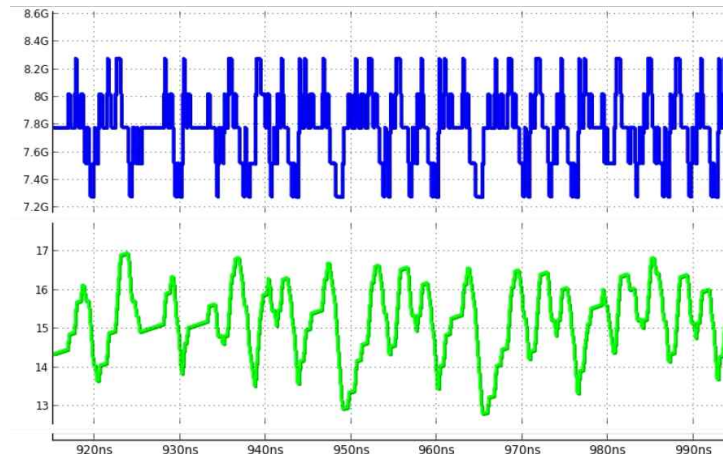

phase


- without STAY signal (K_p, K_i) = (64, 4)

frequency

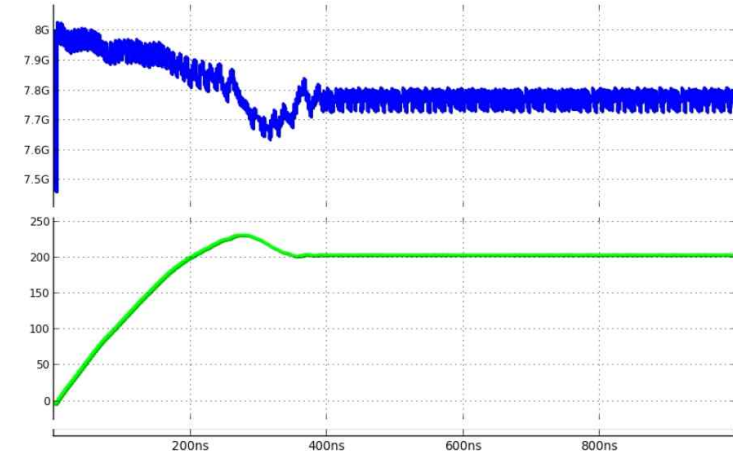

phase

frequency

 


phase

Frequency/Phase of the Recovered Clock

- with STAY signal $(K_p, K_i) : (1024, 1) \Leftrightarrow (64, 4)$

frequency

 

phase

frequency



phase

Phase Dithering Step :

($K_p = 1024$, $K_i = 1$)


> ($K_p = 64$, $K_i = 4$)

≈ Proposing Method

Frequency/Phase of the Recovered Clock

- with STAY signal $(K_p, K_i) : (1024, 1) \Leftrightarrow (64, 4)$

PRBS Data & CLK180 aligned successfully

 

Performance Test

Phase Noise of the recovered clock


CP up/dn current = 51/49uA data rate : 7.77Gb/s

Initial Control Voltage = 0.5V cdr locking time : 2us


Rs = 1.4k ohm, Cs = 7.2pF, Cp = 1.8pF simulation time : 3us

leakage current : 1uA, VCO range : 7GHz ~ 9GHz timescale : 100fs/100fs


- Analog CDR

 

 
- without STAY signal (K_p, K_i) = (64, 4)



 - without STAY signal (K_p, K_i) = (1024, 1)



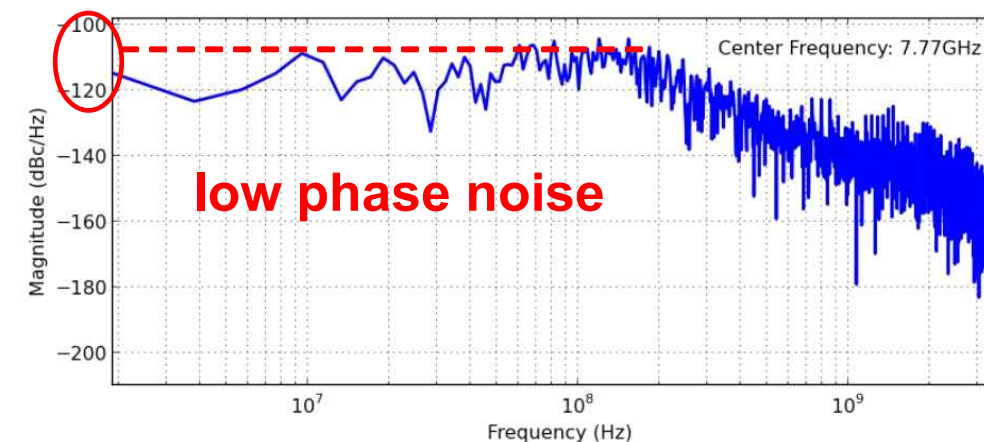- with STAY signal (K_p, K_i) : (1024, 1) \Leftrightarrow (64, 4)



Jitter Histogram of the recovered clock


CP up/dn current = 51/49uA data rate : 7.77Gb/s

Initial Control Voltage = 0.5V cdr locking time : 2us


Rs = 1.4k ohm, Cs = 7.2pF, Cp = 1.8pF simulation time : 3us

leakage current : 1uA, VCO range : 7GHz ~ 9GHz timescale : 100fs/100fs


- Analog CDR

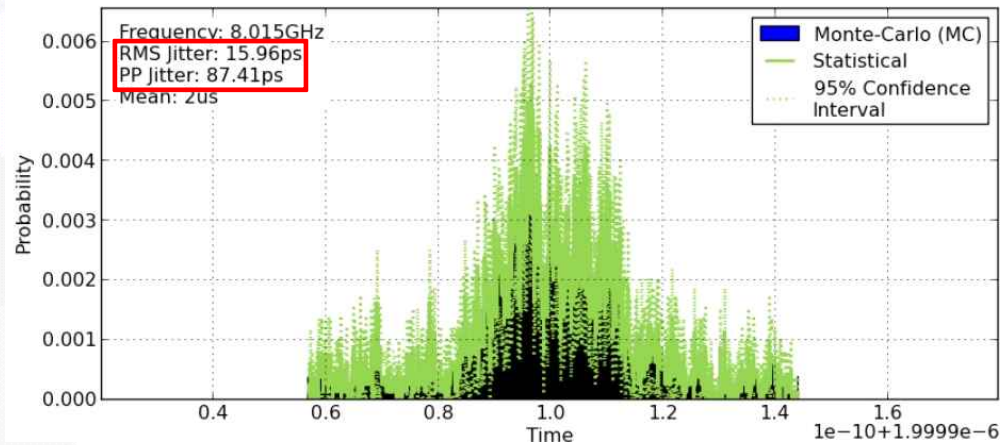

 
- without STAY signal (K_p, K_i) = (64, 4)



 - without STAY signal (K_p, K_i) = (1024, 1)



 - with STAY signal (K_p, K_i) : (1024, 1) \Leftrightarrow (64, 4)



Jitter Tolerance


RJ rms (prbs) : 1ps data rate : 7.77Gb/s

target BER : 1e-9 cdr locking time : 1us


DJ type : Sinusoidal (SJ) simulation time : 10us

SJ freq range : 0.5Mhz ~ 100Mhz timescale : 100fs/100fs

 
- without STAY signal (K_p, K_i) = (1024, 1)



 - without STAY signal (K_p, K_i) = (64, 4)




 - with STAY signal (K_p, K_i) : (1024, 1) \Leftrightarrow (64, 4)




Conclusion

Summarize

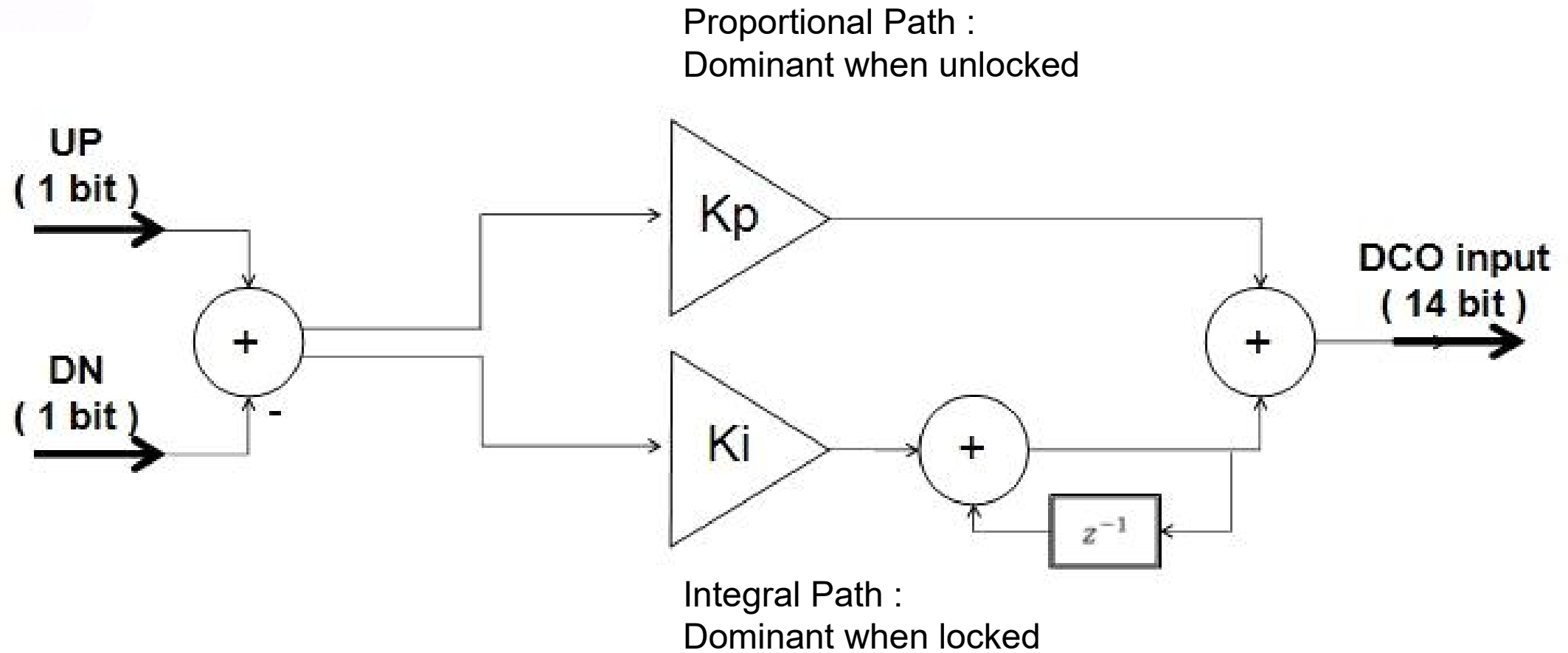

Advantages of Proposed Architecture

Proposing Method

 

data rate :

0~2us : 7.95Gb/s


2~4us : 8.02Gb/s

4~6us : 7.93Gb/s

6~8us : 7.98Gb/s


8~10us : 7.95Gb/s

$K_p = 1024, K_i = 1$

 

Issue : Large Dithering, Jitter Tolerance

$K_p = 64, K_i = 4$

 

Issue : Jitter Peaking, Jitter Tolerance

Q & A